

Total No. of Questions : 10]

SEAT No. :

P1487

[5460]-163

[Total No. of Pages : 2

T.E. (Electrical)

POWER ELECTRONICS

(2012 Course) (Semester - I) (End Semester)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to candidates:

- 1) *Solve questions Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8 and Q9 or Q10.*
- 2) *Assume suitable data, if necessary.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Figures to the right side indicate full marks.*

- Q1)** a) Explain gate characteristics of SCR. [5]
b) Describe the working of single phase half controlled converter with RLE load. Draw neat circuit diagram, and waveforms for [5]
i) Output voltage.
ii) Output current.

OR

- Q2)** a) What are different methods of triggering of SCR? Explain UJT triggering method. [5]
b) Explain working of single phase AC voltage regulator with resistive load. [5]

- Q3)** a) Draw V-I characteristics of TRIAC & explain how it can be used as voltage regulator with suitable example. [5]
b) Explain working of a three phase fully controlled bridge rectifier feeding highly inductive load with help of neat circuit diagram. What is the boundary of discontinuous conduction? Write expression of average output voltage. [5]

OR

- Q4)** a) What is a dual converter? Explain working of Single phase dual converter with suitable diagram to give 4 quadrant operation of a motor. [5]
b) A single phase supply of 230 V, 50 Hz is to deliver power to a load of $R = 10\Omega$ through a half wave controlled rectifier. For a firing angle of 60° , determine : [5]
i) The rectification efficiency.
ii) Form Factor.
iii) Ripple Factor.

P.T.O.

- Q5) a)** Draw and explain switching characteristics of IGBT. [8]
b) Explain the control strategies used in dc choppers to control output voltage. What are the drawbacks of FM control? [8]

OR

- Q6) a)** Explain with neat diagram working of a step up chopper feeding an inductive load. Draw output voltage and current waveforms. Derive average and rms output voltages equations in terms of duty cycle. [10]
b) A step –up chopper has input voltage of 220 V and output of 660 V. If the conduction time of chopper is 100 μ sec, compute the pulse width of output voltage. If the output voltage pulse width is halved for constant frequency operation, find the average value of new output voltage. [6]

- Q7) a)** Explain with neat circuit diagram and waveforms the operation of single phase voltage source inverter feeding RL load. [8]
b) Explain multiple pulse width modulation technique for inverter control. Explain modulation indices and effect on harmonic control. [8]

OR

- Q8) a)** How inverters are classified? What are the external and internal voltage control methods in inverter? [8]
b) Explain sinusoidal pulse width modulation with necessary waveforms. [8]

- Q9) a)** Draw the circuit diagram of three phase inverter feeding resistive load (star connected) using 180° conduction mode. Draw the switching sequence of the devices and waveforms of output phase and line voltages. [10]
b) What is the necessity of controlling the voltage at the output terminals of the inverter? Explain briefly the various methods employed for the control of output voltage of inverters. [8]

OR

- Q10)a)** What are the types of Multilevel Inverter? Explain cascaded multilevel inverter. [10]
b) Compare Multilevel inverter with Multi pulse Inverter. [8]

