

Total No. of Questions :6]

SEAT No. :

P91

[Total No. of Pages :2

APR. -16/TE/InSem. - 23
T.E.(E & TC Engineering)
POWEELECTRONICS
(2012 Pattern) (Semester - II)

Time : 1Hour]

[Max. Marks :30

Instructions to the candidates:

- 1) *Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6.*
- 2) *Neat diagrams and waveforms must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of nonprogrammable calculator is allowed.*
- 5) *Assume suitable data if necessary.*

Q1) a) Draw & explain two transistor analogy of SCR. **[6]**

- b) For an SCR, the gate cathode characteristics has a straight line slope of 130. For triggering source voltage of 15v and allowable gate power dissipation of 0.5W, calculate the gate series resistance(R_g). **[4]**

OR

Q2) a) Draw construction diagram of n-channel enhancement type MOSFET and explain its steady state characteristics. **[5]**

- b) Compare power MOSFET with SCR. **[5]**

Q3) a) Draw & explain single phase fully controlled bridge converter for R-L load with various o/p voltage waveforms. **[7]**

- b) A single phase semi converter is operated from 120V, 50Hz AC supply. The load is resistive having resistance of 15Ω . If the average output voltage is 25% of the maximum possible average output voltage, determine the firing angle(α). **[3]**

OR

Q4) a) Draw & explain three phase half controlled bridge converter for R load with o/p voltage waveforms. **[7]**

- b) Explain the significance of free wheeling diode in controlled rectifiers. **[3]**

P.T.O.

- Q5)** a) Draw & explain single phase full bridge inverter for R-L load with o/p voltage & current waveforms. [6]
- b) Single phase full bridge inverter is operated from 48V dc supply, it has a resistive load of $R = 2.4 \Omega$. Find its. [4]
- i) Output power(P_o)
- ii) Total harmonic distortion(THD)

OR

- Q6)** Explain 120° mode in three phase inverters for balanced star R load with circuit diagram in detail. [10]

