

Total No. of Questions : 8]

SEAT No. :

P3510

[5560]-160

[Total No. of Pages : 2

**T.E. (E&TC Engineering)
POWER ELECTRONICS
(2012 Pattern) (Semester - II)**

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) *Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.*
- 2) *Neat diagrams and waveforms must be drawn wherever necessary.*
- 3) *Use of non-programmable calculator is allowed.*
- 4) *Assume suitable data if necessary.*

- Q1)** a) Draw the steady-state characteristic of SCR and explain all regions. [6]
b) Draw the circuit diagram of single phase Full converter with R load. Explain the circuit operation with neat equivalent circuit diagrams. Sketch the neat waveform for output voltage at firing angle 90° . [7]
c) Draw the circuit diagram of single phase Full Bridge Inverter with R load. Explain the circuit operation with neat equivalent diagrams. Also, sketch the waveform for output voltage. [7]

OR

- Q2)** a) Draw the circuit diagram of synchronized UJT triggering circuit for SCR. Sketch the waveforms of voltage across zener, capacitor and base voltage. Show firing angle α in waveforms. [6]
b) Draw and explain 3ϕ semi-converter with R load. Draw the output voltage waveform. [7]
c) Draw the circuit diagram of 3ϕ inverter with balanced star R load with 180° conduction mode. Explain the operation. [7]

- Q3)** a) Draw the circuit diagram of stepdown chopper. Explain the operation with neat waveforms for i/p and o/p voltages. [6]
b) A DC chopper is operated with resistive load $R = 10\Omega$, input voltage $V_s = 230V$, Determine the average and rms output voltage with duty cycle 50%. [4]
c) Draw the circuit diagram of two quadrant chopper and explain the operation with neat equivalent diagram. [8]

OR

P.T.O.

- Q4)** a) Draw the circuit diagram of single-phase Full Wave AC voltage controller with R load. Explain its operation with neat waveform of output voltage at $\alpha = 90^\circ$. [6]
- b) A step up chopper is operated with R load. $R = 10\Omega$, input voltage $V_s = 100$ V. Determine the average and rms output voltage when duty cycle is 50%. [4]
- c) Draw and explain DC step-up chopper. Sketch the waveform for output voltage. [8]

- Q5)** a) Draw and explain on-line and off-line UPS system. [8]
- b) Write a short note on any two : [8]
- Battery charger.
 - HVDC.
 - Stepper motor control.
 - Induction motor speed control.

OR

- Q6)** a) Draw and explain 1ϕ separately excited DC motor speed control circuits. [8]
- b) Write a short note on any two : [8]
- HVAC.
 - Circuit breaker.
 - UPS system specifications.

- Q7)** a) Draw and explain ZCS resonant converter with neat waveforms and equivalent diagrams. [10]
- b) What is EMI? List sources of EMI and explain its reduction techniques. [6]

OR

- Q8)** a) Explain over voltage and over current protection circuits. [8]
- b) Draw and explain SLR with neat equivalent diagrams and waveforms. [8]

