

Total No. of Questions : 6]

SEAT No. :

P35

[Total No. of Pages : 1

APR-17/B.E./Insem. - 39
B.E. (Electrical Engineering)
HVDC AND FACTS
(2012 Pattern) (Semester - II) (Elective - III)

Time :1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) *Neat diagrams must be drawn wherever necessary.*
- 2) *Figures to the right indicate full marks.*
- 3) *Use of logarithmic tables slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.*
- 4) *Assume suitable data, if necessary.*

- Q1)** a) Explain Graetz circuit. Draw relevant waveforms. [6]
b) Develop equivalent circuit of HVDC link. [4]

OR

- Q2)** a) Compare CIA control and CEA control used in HVDC Systems converter station. [4]
b) Explain effect of delay angle and angle of advance commutation on operation HVDC system. [6]

- Q3)** a) Give typical layout of HVDC system. [5]
b) Draw schematics of multi-terminal HVDC systems and state applicability of each. [5]

OR

- Q4)** a) State advantages of multi-terminal HVDC with classical HVDC system. [4]
b) What is single wire ground return system? Which configuration is commonly employed in such system? [6]

- Q5)** a) Discuss the operation of VSC based HVDC system. [5]
b) Explain structure of VSC based HVDC system. [5]

OR

- Q6)** a) Compare Classical HVDC system with VSC based HVDC system. [7]
b) Explain Power transfer Characteristics of VSC HVDC System. [3]

▽▽▽▽