

Total No. of Questions—8]

[Total No. of Printed Pages—6

Seat No.	
-------------	--

[5152]-133

S.E. (E&TC/Electronics) (I Sem.) EXAMINATION, 2017

NETWORK THEORY


(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50


- N.B. :-**
- (i) Neat diagrams must be drawn wherever necessary.
  - (ii) Figures to the right indicate full marks.
  - (iii) Your answers will be valued as a whole.
  - (iv) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
  - (v) Assume suitable data, if necessary.

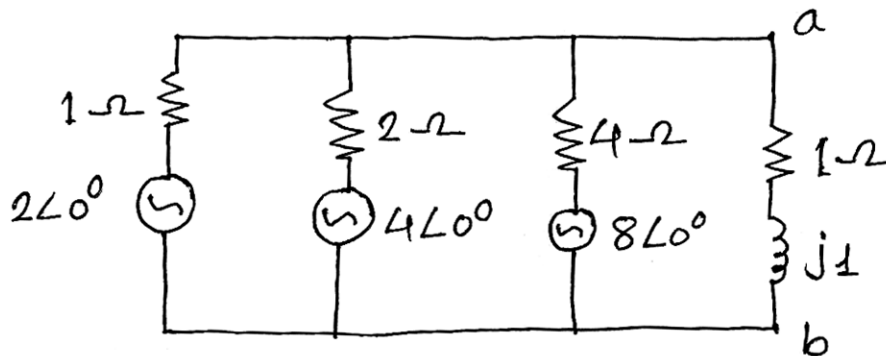1. (a) Find the current passing through the impedance  $(1 + j1)$  in the circuit shown below, using Nortons theorem. [6]




P.T.O.

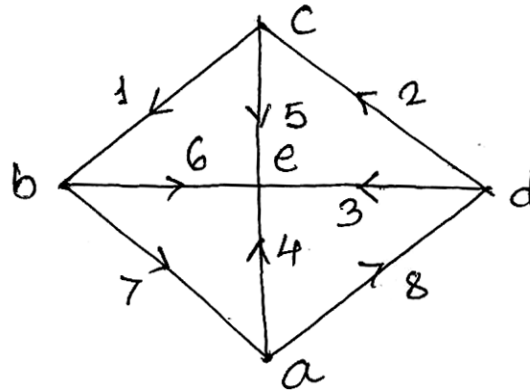- (b) What is meant by oriented graph ? Find the voltage drop equations for the oriented graph shown below. [6]



Or

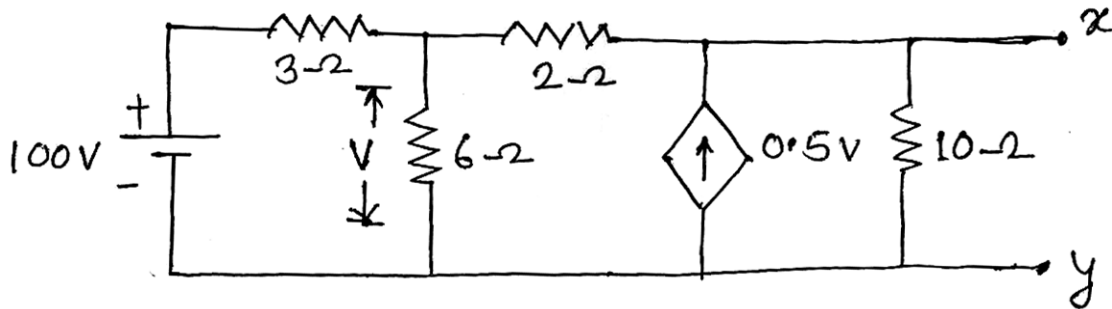
2. (a) State Norton's theorem and find the Norton's equivalent circuit at the terminals  $xy$  of the circuit shown below. [6]



- (b) Explain the tree with example and determine the possible numbers of tree of a incidence matrix  $[A]$  of a graph is given by : [6]

$$[A] = \begin{bmatrix} -1 & 0 & 0 & 1 \\ 1 & -1 & 1 & 0 \\ 0 & 1 & -1 & -1 \end{bmatrix}_{3 \times 4}$$

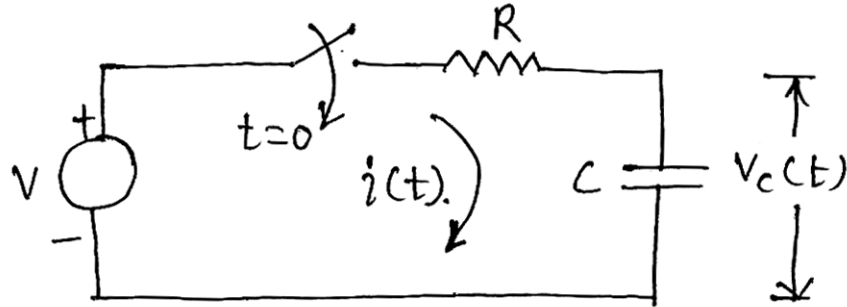
3. (a) Derive the expression for voltage across the capacitor and current flowing through it of circuit shown below : [6]




- (b) For a parallel resonant circuit, find :
- (i) Specify the value of the circuit capacitor
  - (ii) Resistance of the circuit at parallel resonance
  - (iii) What is the absolute bandwidth of the resonant circuit ?
  - (iv) The bandwidth of the circuit, when it is matched with the generator impedance.
- When  $Q = 75$ ,  $L = 120 \mu\text{H}$  and resonating frequency of 1 MHz. [6]

*Or*

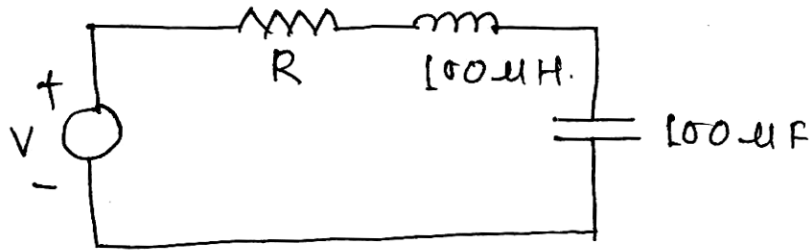
4. (a) The series resonant circuit has a lagging phase angle of  $30^\circ$  at  $\omega_H = 12000 \text{ rad/sec}$ . at what frequency will be leading by  $30^\circ$ . [6]



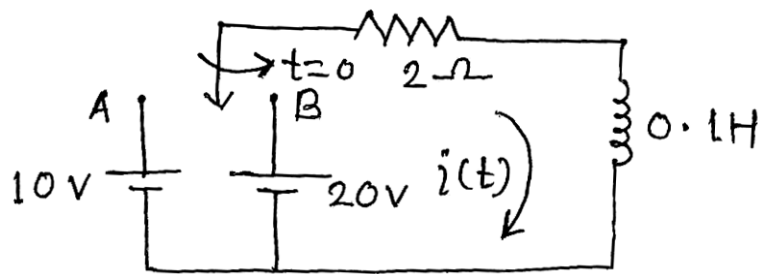- (b) The circuit shown below find, the current flowing through the inductor, when switch is at position 'A' and 'B'. [6]




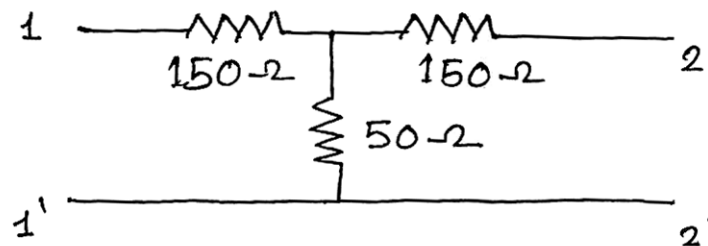5. (a) Design a HPF, 'T' and 'π' section to work into impedance  $500 \Omega$ , and have a cut-off frequency of 1 kHz. For this, calculate the phase angle  $\beta$  at frequency 1.5 kHz and attenuation  $\alpha$  in neper at frequency of 0.9 kHz. [7]
- (b) A symmetrical 'T' attenuator shown below. Find OC & SC impedance,  $Z_0$ . attenuation constant in dB : [6]



Or

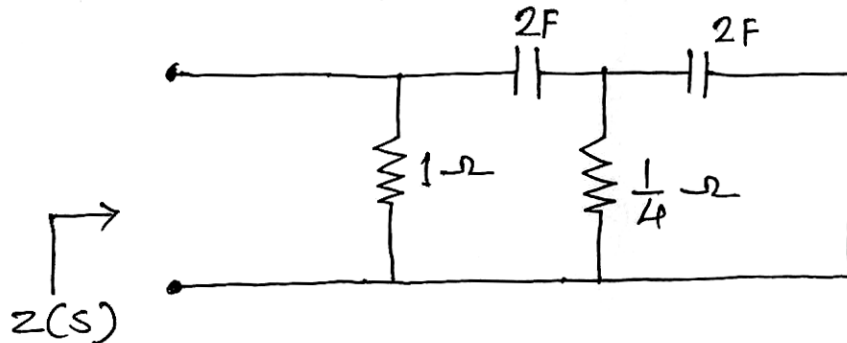6. (a) Design a constant 'K'  $\Pi$  section HPF to have a design impedance of  $600 \Omega$ . The filter must have attenuation of 8.11 dB at 4.5 kHz and for this design calculate, phase angle in degree at frequency 5.5 kHz. [6]
- (b) Find the image and iterative impedance for the asymmetrical 'L' section whose series arm impedance is  $400 \Omega$  and shunt arm impedance is  $600 \Omega$ . Derive the formula used. [7]
7. (a) What is meant by poles and zeros ? For the network shown below find the  $Z(s)$  : [7]



- (b) The Z-parameter of a circuit are given by : [6]

$$\begin{bmatrix} 4 & 1 \\ 3 & 3 \end{bmatrix}$$

Obtain the transmission parameters.

Or

8. (a) Derive the condition of Reciprocity and symmetry for the ABCD parameter. [6]
- (b) Determine the 'Y' parameters for the Network. [7]

