

Total No. of Questions—8]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[5352]-133

S.E. (E&TC/ELECTRONICS) (I Sem.) EXAMINATION, 2018

NETWORK THEORY


(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

- N.B.* :— (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.
(ii) Figures to the right indicate full marks.
(iii) Assume suitable data, if necessary.

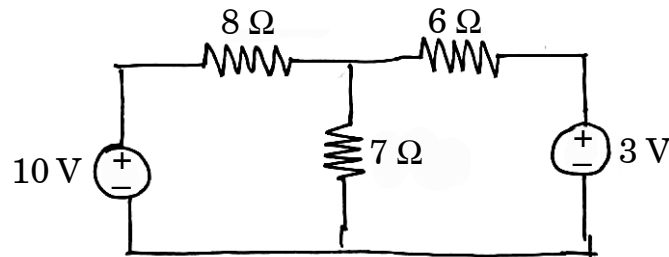1. (a) For the network shown below, find current through 7Ω resistor using superposition theorem. [6]




- (b) Explain the following terms with example : [6]
- (i) Oriented graph
 - (ii) Rank of graph
 - (iii) CoTree
 - (iv) Twig.


P.T.O.

Or

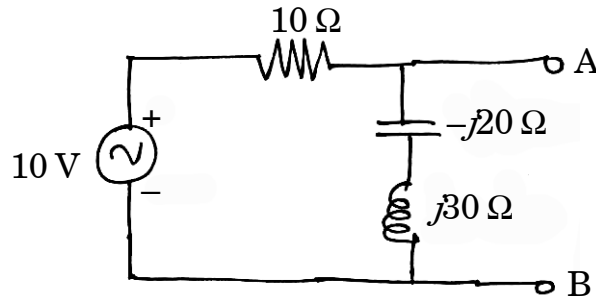
2. (a) Obtain Thevenin's equivalent circuit w.r.t. points A & B for the circuit below : [6]



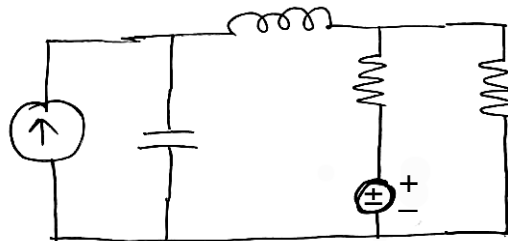- (b) Find the maximum possible number of trees for the network shown in Fig. [6]



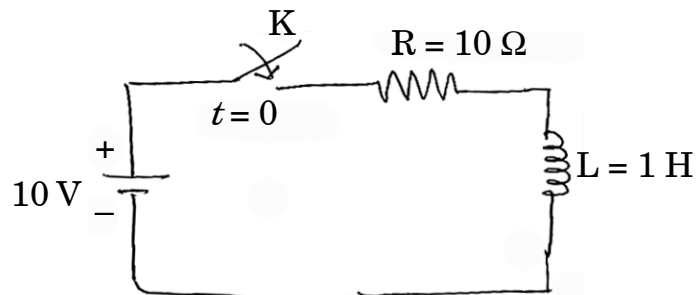
3. (a) The switch is closed at $t = 0$. Find value of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$. Assume initial current of inductor to be zero. [6]



- (b) An inductive coil having resistance of 50Ω and inductance of 0.05 H is connected in series with $0.02 \mu\text{F}$ capacitor. Find : [6]
- (i) Q factor of coil
(ii) Resonant frequency
(iii) Half power frequency.

Or

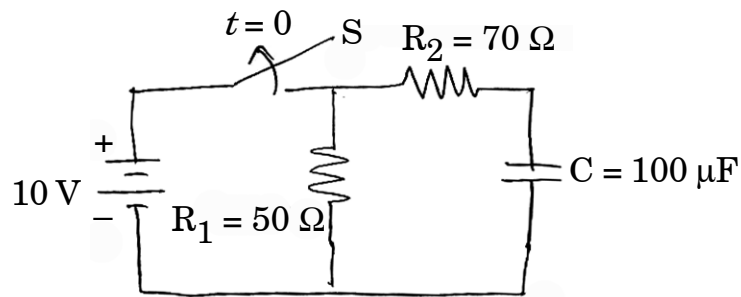
4. (a) In Fig., the switch 'S' is opened at $t = 0$. Find the expression for voltage across C for $t > 0$. Also find voltage at $t = 0.036 \text{ sec}$. [6]



- (b) Define Q-factor and derive equations for Q-factor of L&C. [6]
5. (a) For any symmetrical network, prove that the characteristic impedance z_0 is the geometric mean of open and short circuit impedances. [6]
- (b) Design constant K-HPF having cut-off frequency 5500 Hz and design impedance of 750Ω . Draw : [7]
- (i) T-section
(ii) π -section.

Or

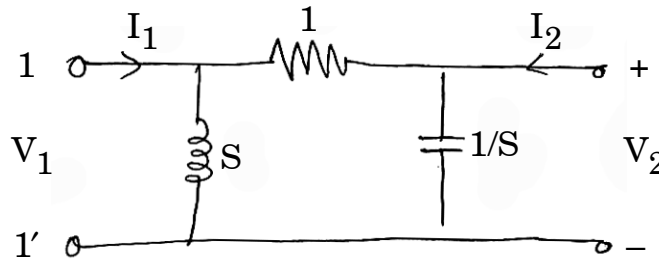6. (a) Design a symmetrical π attenuator to work into 600Ω and provide a loss of 20 dB. [6]
- (b) What are the limitations of prototype filters ? How these limitations are overcome using m -derived filters ? Explain composite filters with its block diagram. [7]
7. (a) Derive the condition of reciprocity and symmetry for z parameters. [6]
- (b) Determine the transmission parameters for the network shown in Fig. [7]



Or

8. (a) Current I_1 and I_2 entering at port 1 and port 2 respective of two port network are given by the following equations :
- $$I_1 = 0.5V_1 - 0.2V_2$$
- $$I_2 = 0.2V_1 + V_2.$$
- Find z parameters. [7]
- (b) Write a short note on : Pole-zeros of network functions and stability. [6]