

Seat No.	
-------------	--

[5252]-133

S.E. (E&TC/Electronics) (I Semester) EXAMINATION, 2017

NETWORK THEORY

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6, Q. 7 or Q. 8.

(ii) Figures to the right indicate full marks.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Assume suitable data if necessary.

(v) Use of non-programmable calculator is permitted.

1. (a) Determine V_x in the circuit of Fig. 1, using Kirchoff's laws.[6]

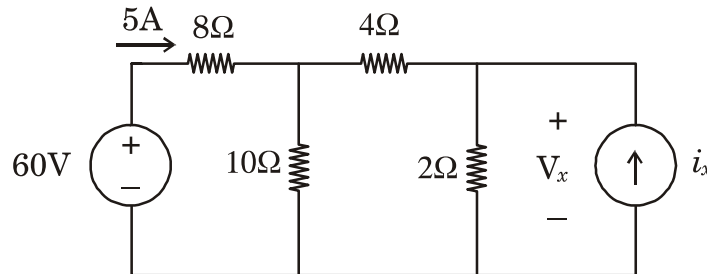


Fig 1.

(b) Draw the dual of the network shown in Fig. 2. [6]

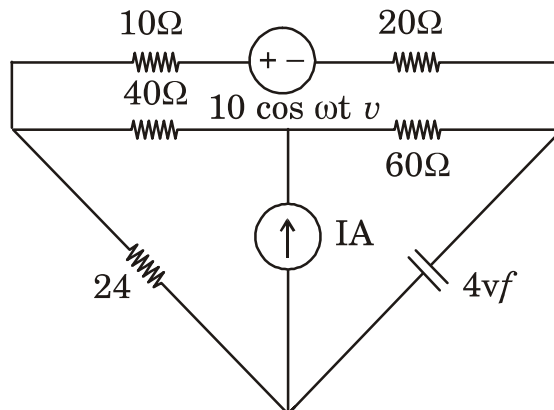


Fig.2

P.T.O.

Or

2. (a) Determine the Thevenin equivalent of the network shown in Fig 3. [6]

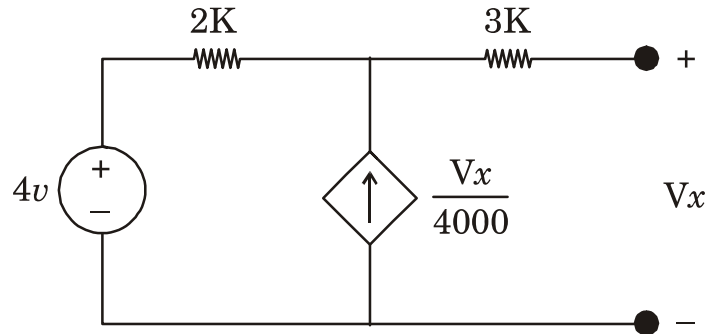


Fig. 3

- (b) For the oriented graph shown in Fig. 4. Determine the Tieset matrix and f -cutset matrix. [6]

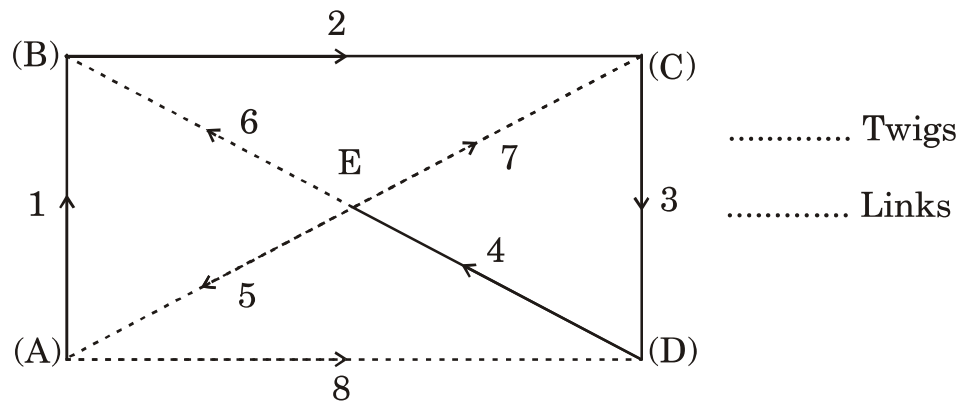


Fig. 4

3. (a) The switch is opened at $t = 0$ for the network shown in Fig. 5, Find voltage labeled V at $t = 200$ ms and also plot $V(t)$. [6]

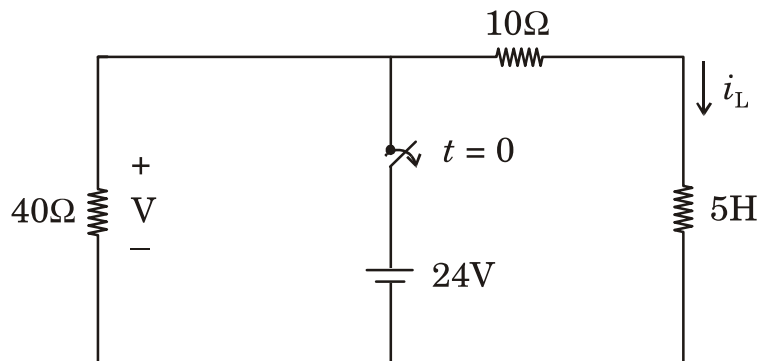


Fig. 5

- (b) A series RLC circuit consists of $R = 100 \Omega$, $L = 0.02 \text{ H}$ and $C = 0.02 \mu\text{f}$. Calculate frequency of resonance. Calculate voltage across L and C at frequency of resonance. Also find maximum current in the circuit. [6]

Or

4. (a) In the circuit shown in Fig. 6, the switch is changed from position 1 to 2 at $t = 0$. Determine initial conditions of i , di/dt , d^2i/dt^2 at $t = 0^+$. [6]

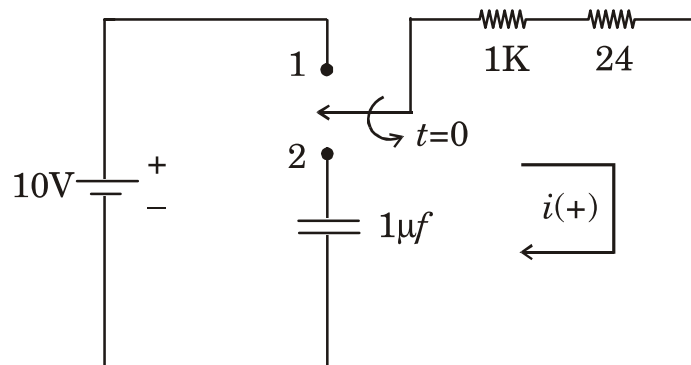


Fig.6

- (b) Explain the variation of voltage across R, L and C on graph with frequency at resonance. Also write the equation of frequencies at which voltage across C and L are maximum. [6]
5. (a) If the measurements made on a box enclosing a two-port network are $Z_{loc} = 40 \angle 0^\circ \Omega$, $Z_{lsc} = 22.3 \angle 29.8^\circ \Omega$. Find the values of characteristic impedance and propagation constant along with attenuation constant and phase constant, if the network is symmetrical. [7]
- (b) Design a constant k high pass π section filter to have a design impedance of 600Ω . The filter must have attenuation of 8.11 dB at 4.5 KHz. Also calculate phase angle at $f = 5.5 \text{ kHz}$. [6]

Or

6. (a) Design m -derived T section LPF having cutoff frequency of 5 KHz and impedance of 600Ω . The frequency of infinite attenuation is 1.25 times the cutoff frequency. [7]
- (b) Define attenuation in Neper and Decibel. Derive the relationship between Neper and Decibel. [6]
7. (a) Find Z parameters for the network shown in Fig. 7 [6]

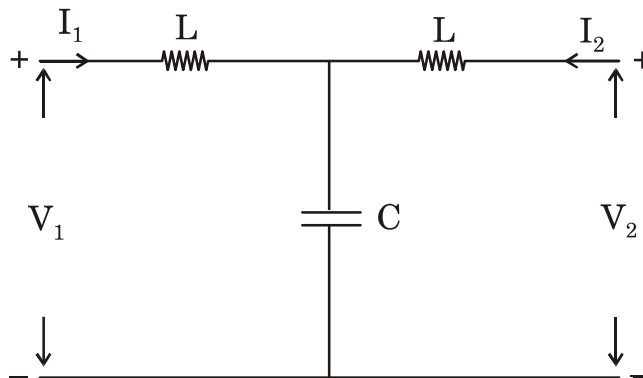


Fig. 7

- (b) Find the driving point admittance $Y(s)$ for the network shown in Fig.8. Also plot pole zero diagram. [7]

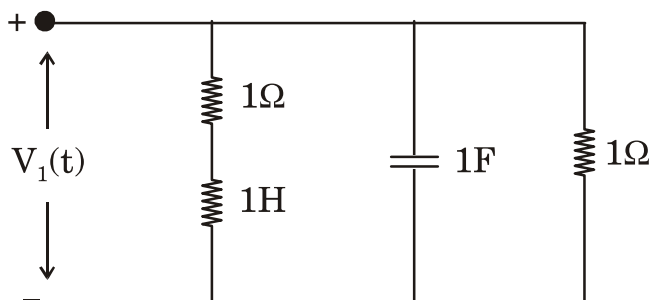


Fig. 8

Or

8. (a) Define symmetrical network. Derive expression for condition of symmetry for T parameter. [6]
- (b) Determine hybrid parameters for the network shown in Fig. 9. [7]

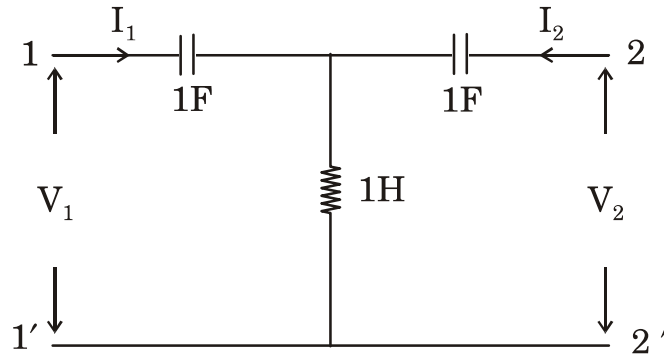


Fig. 9