

Total No. of Questions—8]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[5459]-135

S.E. (E & TC/Electronics) (I Sem.) EXAMINATION, 2018

NETWORK THEORY

(2012 PATTERN)

Time : Two Hours


Maximum Marks : 50

N.B. :— (i) Answer Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4, Q. No. 5 or Q. No. 6 and Q. No. 7 or Q. No. 8.

(ii) Figures to the right indicate full marks.

(iii) Assume suitable data, if necessary.

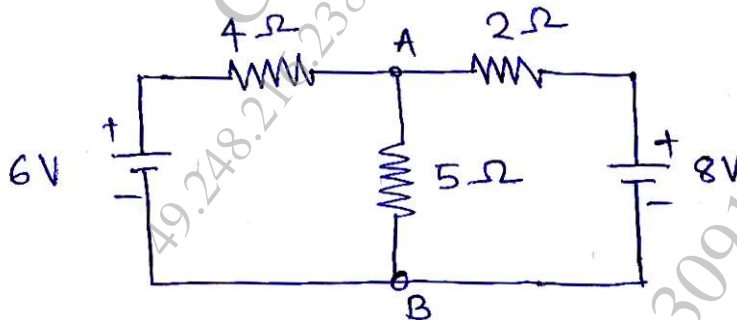1. (a) Find current through branch AB using Thevenin's theorem. [6]



(b) Explain the following terms with example : [6]

(i) Oriented graph

(ii) Tieset matrix


(iii) F-cutset matrix.

P.T.O.


2. (a) State and explain maximum power transfer theorem. [6]
 (b) The reduced incidence matrix is : [6]

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

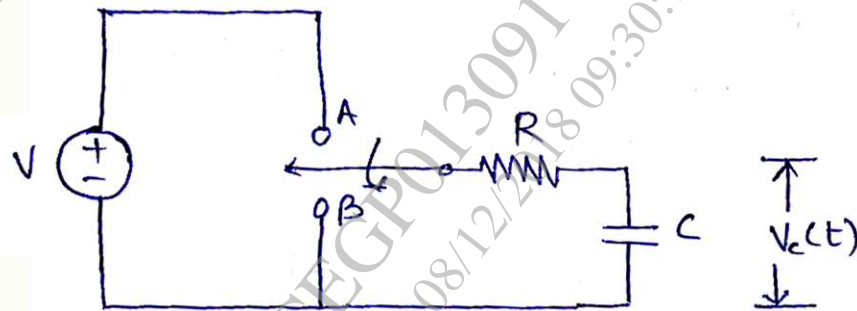
- (i) Obtain complete incidence matrix.
 (ii) No. of trees possible.
3. (a) Derive the expression for the voltage $V_c(t)$ across capacitor for the series RC circuit shown. [6]



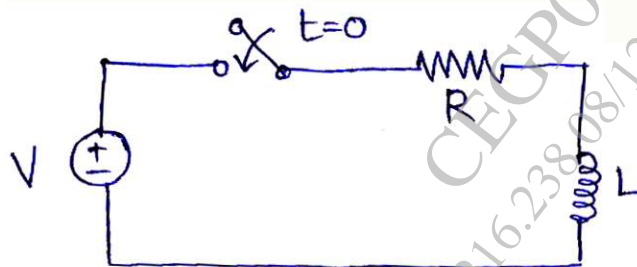- (b) Define the term quality factor. Prove for a series RLC resonant circuit $f_0 = \sqrt{f_1 f_2}$. [6]
4. (a) For the circuit shown below, find the current $i(t)$ for all time $t > 0$. [6]




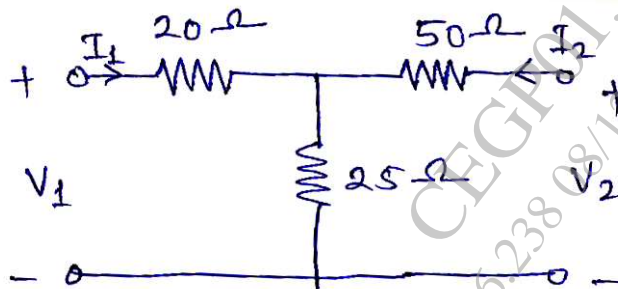- (b) A series resonant circuit has a bandwidth of 100 Hz and contains a 20 mH inductance and a 20 μ f capacitance. Determine : [6]
- f_0
 - Q_0 and
 - Impedance Z at resonance.
5. (a) What is symmetrical network ? Explain *two* characteristics of symmetrical network. [6]
- (b) Design a constant K T type low pass filter with the following specifications : [7]
 Design resistance $R_0 = 560 \Omega$ and
 Cut-off frequency $f_c = 2$ KHz.
6. (a) Design symmetrical T attenuator with attenuation of 20 dB and design resistance of 600 Ω . [6]
- (b) A symmetrical T network is composed of pure resistance has the following values of open and short circuit impedance :
 $Z_{oc} = 800 \Omega$ $Z_{sc} = 600 \Omega$
 Determine characteristic impedance z_0 , z_1 and z_2 for the T network. [7]
7. (a) Find z -parameters for the two port network shown below. State whether the network is symmetrical/asymmetrical. [7]



(b) Find the condition of symmetry and reciprocity of Y parameters. [6]

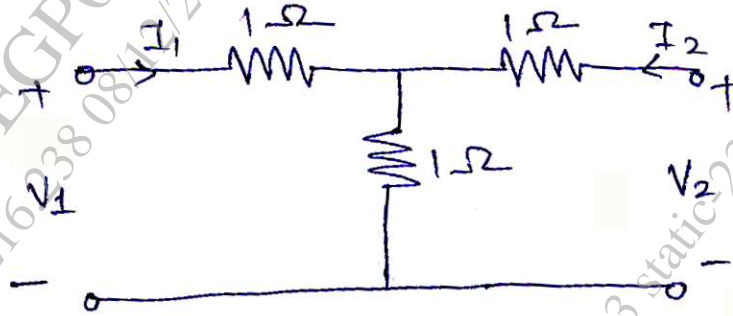8. (a) Find h -parameters for the n/w shown in fig. [6]



(b) Explain the applications of Laplace Transforms to circuit analysis. [7]