

Total No. of Questions : 8]

SEAT No. :

P3102

[Total No. of Pages : 2

[5670]-201
B.E. (E & TC)
VLSI Design and Technology
(2012 Pattern)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) *Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.*
- 2) *Figures to the right indicate full marks.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Assume suitable data, if necessary.*

- Q1)** a) Explain Data Objects in VHDL. [6]
b) Write the features, specifications and applications of CPLD. [7]
c) Write VHDL code and test bench for D FlipFlop. [7]

OR

- Q2)** a) Explore any four attributes in VHDL with suitable example codes. [6]
b) Draw and explain the CLB structure of FPGA device. [7]
c) Explain clock distribution techniques in detail. [7]

- Q3)** a) Explain static and dynamic power dissipation with suitable mathematical expressions. [8]
b) Draw NAND, NOR, EX-OR gates and 2:1 MUX using CMOS. [10]

OR

- Q4)** a) Draw CMOS inverter and explain VTC in detail. [10]
b) Explain need for transmission gate. Draw 4:1 MUX using TG. [8]

- Q5)** a) With the help of equivalent circuit explain MOS as diode and resistor. [8]
b) Write short note on "Cascade Amplifier". [8]

OR

P.T.O.

- Q6)** a) Draw and explain current mirror circuits. [8]
b) Draw and explain current source and sink circuits. [8]

- Q7)** a) Explain TAP controller with state diagram. [8]
b) Explain IEEE 1149.1 architecture. [8]

OR

- Q8)** a) Explain different fault models. [8]
b) Explain boundary scan architecture. [8]

