



C09-EC-306

3238

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH / APRIL - 2019

DECE - III SEMESTER EXAMINATION

CIRCUIT THEORY

Time : 3 Hours]


[Total Marks : 80

PART - A

3×10=30

- Instructions :**
- (1) Answer **ALL** questions.
  - (2) Each question carries **THREE** marks.
  - (3) Answer should be brief and straight to the point.

- 1 Write the expression for the resonant frequency of the following parallel circuits.  
(a) L, C (b) RL, C (c) L, CR
- 2 A sinusoidal signal of 5KHz frequency is applied across a  $0.01 \mu\text{F}$  capacitor. Determine the capacitive reactance.
- 3 State the difference between active and passive circuit elements.
- 4 Determine the number of mesh equations required to solve the network shown below.

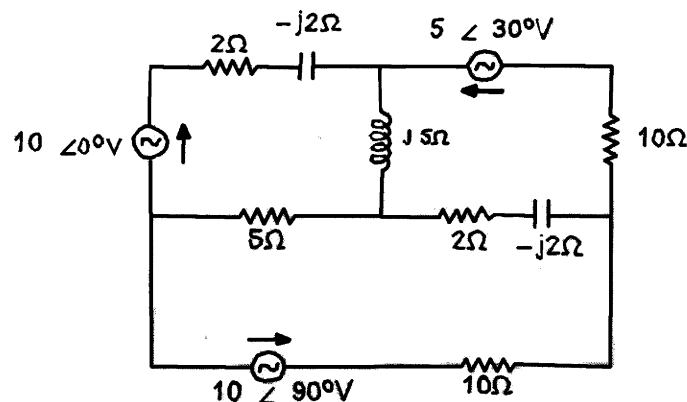


3238 ]

1

[ Contd...

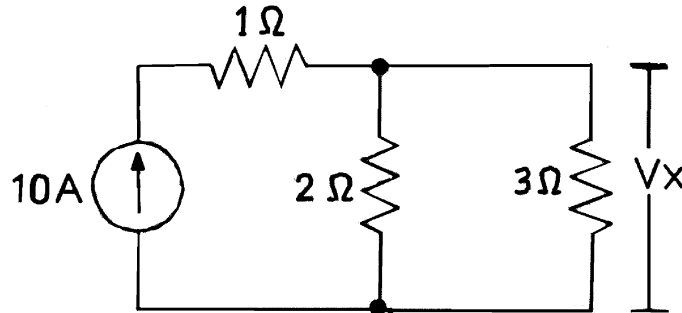- 5 Define driving point impedance and transfer impedance of a network.
- 6 Verify the reciprocity theorem in the circuit shown in figure below :




- 7 List the limitations of Thevenin's theorem.
- 8 Write the expressions for the following parameters of low pass RC circuit.
  - (i) Upper 3dB frequency
  - (ii) Rise time in terms of upper 3dB frequency
- 9 Define :
  - (a) Co-efficient of coupling
  - (b) Critical coupling
- 10 Define reflected impedance of a coupled circuit.

**PART - B**

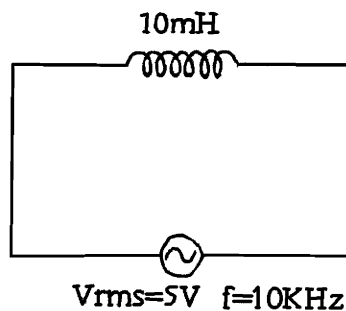
**10×5=50**

- Instructions :**
- (1) Answer any **FIVE** questions.
  - (2) Each question carries **TEN** marks.
  - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.


- 11 (a) Explain V-I characteristic of a pure inductor with a.c.source.
- (b) Determine the r.m.s. current in the circuit shown below :



- 12 (a) Distinguish between series and parallel resonance.
- (b) Find the value of inductance which should be connected in series with a capacitor of  $5 \mu\text{F}$  and resistor of  $100 \Omega$  and an a.c. source of  $50 \text{ Hz}$  so that power factor of the circuit is unity.
- 13 In the following figure a balanced delta connected circuit with  $Z = 10 \angle 30^\circ \Omega$  is parallel with a balanced star connected circuit with  $Z = 4 \angle 45^\circ \Omega$ . Obtain the star connected equivalent,

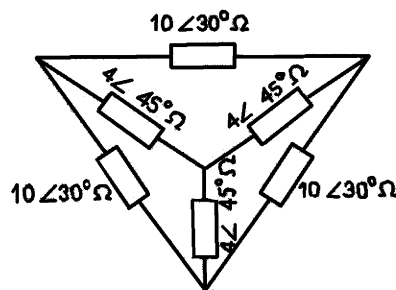


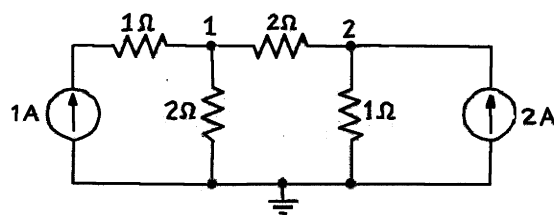- 14 Determine the voltages at nodes 1 and 2 of the network shown below by using input and transfer admittances,




- 15 (a) Explain ideal voltage source and ideal current source. 4
- (b) A constant current source develops a terminal voltage of  $9 \text{ V}$  when a  $500 \Omega$  resistor is connected across its terminals. What is its terminal voltage when the  $500 \Omega$  resistor is replaced by a  $1.5 \text{ K}\Omega$  resistor ? 6

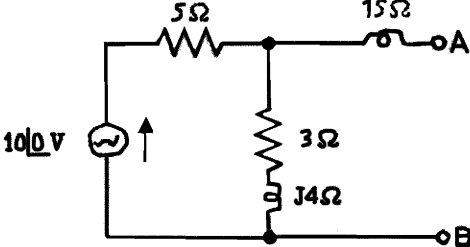16 Obtain Norton equivalent circuit at the terminals A, B for the circuit shown in figure,



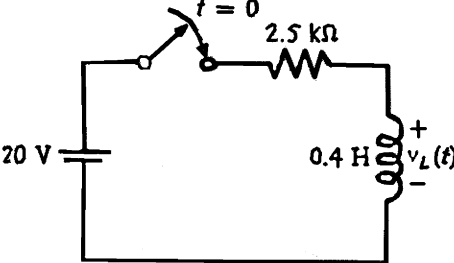17 At what time after the switch is closed in the following figure does  $V_1(t)$  reach 15 V,



18 For the circuit shown below :

- (a) Find the time constant
- (b) After how many time constants will the current have decayed to one-half its maximum value ?

