



C09-EE-306

3244

BOARD DIPLOMA EXAMINATION, (C-09)

MARCH / APRIL - 2019

DEEE– III SEMESTER EXAMINATION

ELECTRONICS ENGINEERING

Time : 3 Hours]

[Total Marks : 80

PART - A

3×10=30

- Instructions :**
- (1) Answer **ALL** questions.
 - (2) Each question carries **THREE** marks.
 - (3) Answer should be brief and straight to the point.

- 1 State the need for a filter in power supplies.
- 2 Draw the regulation characteristics of a Zener diode.
- 3 Briefly explain the working principle of UJT.
- 4 List the applications of LCD.
- 5 Write the applications of photo diode.
- 6 Define stability factor.
- 7 Classify amplifiers based on frequency.
- 8 Define the terms gain and decibel gain of an amplifier.
- 9 Classify oscillators based on components used.
- 10 State the need for an industrial timer.

3244]

1

[Contd...

PART - B**10×5=50**

- Instructions :**
- (1) Answer any **FIVE** questions.
 - (2) Each question carries **TEN** marks.
 - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11 Explain bridge rectifier using LC filter with waveforms.
 - 12 (a) Explain the construction and working of solar cell. 7
(b) Write the applications of optocoupler. 3
 - 13 (a) Explain how transistor works as an amplifier.
(b) Write the causes of instability of biasing in transistor amplifier.
 - 14 Explain the effect of feedback on gain bandwidth, distortion and noise in amplifiers.
 - 15 Explain the working principle of complementary push pull power amplifier.
 - 16 Briefly explain the use of OPamp as an Inverter and Summing amplifier.
 - 17 Draw and explain the working of crystal oscillator.
 - 18 Draw and explain the block diagram of a function generator.
-