



C-09-EE-405

**3477**

**BOARD DIPLOMA EXAMINATION, (C-09)**

MARCH / APRIL - 2019

**DEEE - IV SEMESTER EXAMINATION**

**DIGITAL ELECTRONICS & MICRO CONTROLLERS**

Time : 3 Hours]

[Total Marks : 80

**PART - A**

**3×10=30**

- Instructions :**
- (1) Answer **ALL** questions.
  - (2) Each question carries **THREE** marks.
  - (3) Answer should be brief and straight to the point.
- 1 Explain how a bubbled AND gate is equivalent to a NOR gate with symbols and truth tables.
  - 2 Draw the logic circuit and truth table of 2×4 decoder.
  - 3 Distinguish between flash ROM and NVRAM.
  - 4 What is a shift register ? List the different types of shift registers.
  - 5 List the alternate functions of port 3 of 8051 microcontroller.
  - 6 What is the difference between a Counter and a Timer ?
  - 7 List any six conditional jump instructions of 8051 microcontroller.
  - 8 State the addressing mode of each of the following instructions :
    - (a) MOV A, #30 H
    - (b) MOV A, @R0
    - (c) SUBB A, 56 H
    - (d) MOVX A, @DPTR
    - (e) RR A
    - (f) ADD A, R1.
  - 9 Define machine cycle and instruction cycle.
  - 10 Draw a flow chart to multiply two numbers 56H and 33H.

3477]

1

[ Contd...

## PART - B

10×5=50

- Instructions :**
- (1) Answer any **FIVE** questions.
  - (2) Each question carries **TEN** marks.
  - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11 Perform the following conversions : 4+4+2
- (a)  $125_{10}$  into Binary and Octal number systems.
  - (b)  $AC6.F3_{16}$  into Binary and Decimal number system.
  - (c)  $1010111_2$  into BCD.
- 12 Draw the circuit and explain the working of 4 bit parallel binary adder with an example.
- 13 Draw the diagram and explain the working of 4-bit asynchronous counter with truth table and wave forms.
- 14 Draw the circuit and explain the operation of master slave JK flipflop.
- 15 Draw and explain the bit wise description of IE and IP registers.
- 16 Explain the register structure of 8051 microcontroller.
- 17 (a) Explain RR A and RRC A instructions with one 5+5  
example.
- (b) Explain the following instructions :
- (i) DA A
  - (ii) MUL AB.
- 18 Write an assembly language program along with comments to add two 8-bit numbers stored in the external memory locations 4500H and 4501 H. Store the result at 4502H and 4503H.