



C14-EC-306

4241

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH / APRIL - 2019

DECE - III SEMESTER EXAMINATION

ELECTRICAL TECHNOLOGY

Time : 3 Hours]

[Total Marks : 80

PART - A

3×10=30

Instructions :

- (1) Answer **ALL** questions.
- (2) Each question carries **THREE** marks.
- (3) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1 Draw the vector diagram of a series R-L circuit.
- 2 Compare series and parallel resonance.
- 3 List out various parts of a DC generator.
- 4 What is the significance of back emf in a DC motor ?
- 5 List out various losses in a DC machine.
- 6 What are the advantages of a polyphase system over single phase system ?
- 7 Define coefficient of coupling.
- 8 Classify the transformers.
- 9 Write an emf equation of alternator and mention the units of each parameter.
- 10 Define slip and slip speed.

4241]

1

[Contd...

PART - B

10×5=50

- Instructions :**
- (1) Answer any **FIVE** questions.
 - (2) Each question carries **TEN** marks.
 - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11** A resistance of 12Ω , an inductance of 0.15H and a capacitance of $100\mu\text{f}$ are connected in series across 100V , 50Hz supply. Calculate :-
- (i) Impedance
 - (ii) Current
 - (iii) Power factor
 - (iv) Power consumed
- 12** Derive the expression for resonant frequency in a series RLC circuit.
- 13** Two impedances $Z_1 = (6 + j8)$ and $Z_2 = (8 - j6)$ are connected in parallel. Calculate the total (a) conductance (b) susceptance (c) admittance and (d) current taken from the supply and its p.f. if the supply voltage is 200V , 50Hz .
- 14** Derive an emf equation of a DC generator.
- 15** Explain with a circuit the working of a three point starter.
- 16** A balanced three phase delta connected load has per phase impedance of $(25 + j40)\Omega$. If 400V 3-phase supply is connected to this load, find
- (i) Phase current
 - (ii) Line current
 - (iii) power supplied to the load.
- 17** Explain the construction and working of an auto transformer.
- 18** Explain the working principle of a synchronous motor.