



C14-EC-402

4435

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH / APRIL - 2019

DECE - IV SEMESTER EXAMINATION

LINEAR INTEGRATED CIRCUITS

Time : 3 Hours]

[Total Marks : 80

PART - A

3×10=30

Instructions :

- (1) Answer **ALL** questions.
- (2) Each question carries **THREE** marks.
- (3) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1 List the advantages of integrated circuits over discrete circuits.
- 2 Draw the circuit of first order active Low Pass Filter using op-amp.
- 3 List the characteristics of ideal operational amplifier.
- 4 Define Input offset voltage and Input offset current of operational amplifier.
- 5 Distinguish between voltage and current time base generators.
- 6 Mention the merits of active filters.
- 7 What is the principle of clamping circuit ?
- 8 Define Lock range of PLL.
- 9 List the applications of current to voltage converter.
- 10 Define the terms resolution and accuracy.

4435]

1

[Contd...

PART - B

10×5=50

- Instructions :**
- (1) Answer any **FIVE** questions.
 - (2) Each question carries **TEN** marks.
 - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11 Explain the fabrication of diode on monolithic IC.
- 12 Explain the use of operational amplifier as differentiator and integrator with neat circuits.
- 13 Draw and explain the working of Schmitt trigger circuit using operational amplifier.
- 14 Draw and explain the RC phase shift oscillator circuit using op-amp.
- 15 (a) Explain the operation of fixed voltage regulator using 78XX series.
(b) Explain the operation of adjustable voltage regulator LM317.
- 16 (a) Explain the frequency multiplier using PLL.
(b) Explain the FM demodulator using PLL.
- 17 Explain the operation of A/d converter using successive approximation method.
- 18 Draw and explain the instrumentation amplifier using three op-amps. Mention the advantages of instrumentation amplifier.