



C14-EC-403

4436

BOARD DIPLOMA EXAMINATION, (C-14)
MARCH/APRIL—2018
DECE—FOURTH SEMESTER EXAMINATION
NETWORK ANALYSIS

Time : 3 hours]


[Total Marks : 80

PART—A

3×10=30


- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

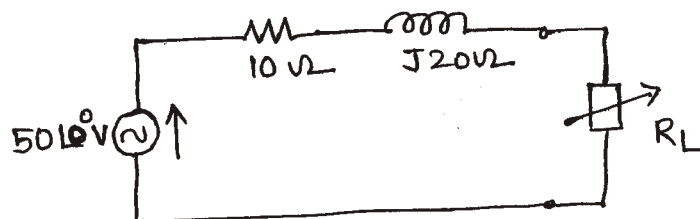1. Write the differences between active elements and passive elements.
2. Explain DOT rule for coupled circuits.
3. State reciprocity theorem.
4. Determine the value of R_L for which the source delivers maximum power to the load R_L in the circuit diagram given below :



5. Define the terms Tree, Co-Tree and Links.

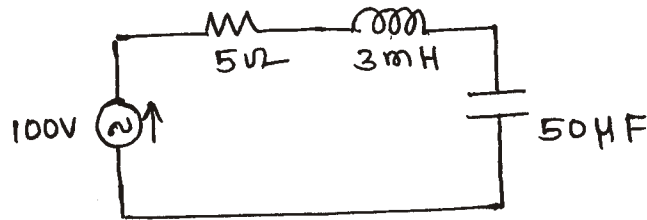6. Draw the dual network for the given series network :



7. Define the terms 'steady-state' and 'transient'.
8. Write the conditions for symmetry and reciprocity in terms of Z , Y , h , $ABCD$ parameters.
9. Define the terms characteristic impedance and propagation constant.
10. Design a simple T-type high-pass filter having cutoff frequency of 1 kHz to operate with a terminated load resistance of 600 Ω .

PART—B


10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.


(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

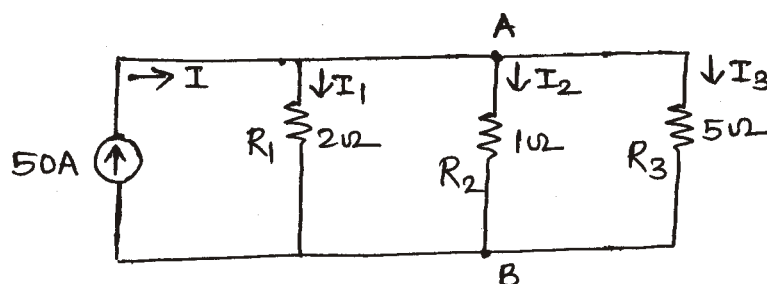11. (a) Explain ideal voltage source and ideal current source. 4
- (b) Determine the currents in all resistors in the circuit shown below, using KCL : 6



12. (a) ^{*} Draw the Thevenin's equivalent network at terminals AB of the given network :

7

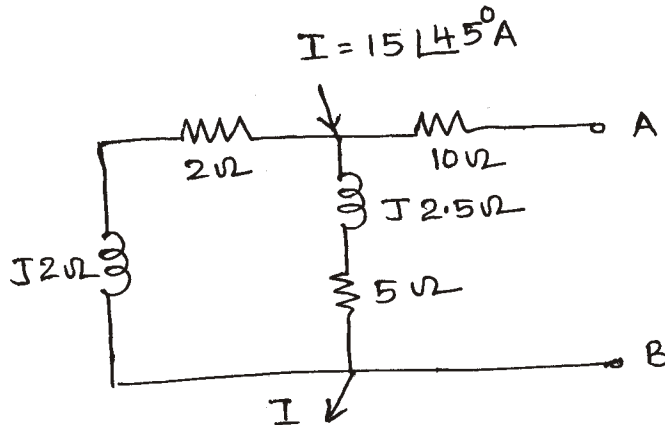


- (b) List the advantages of Norton's theorem.

3


13. (a) Convert the given star-network in to an equivalent delta-network :

5

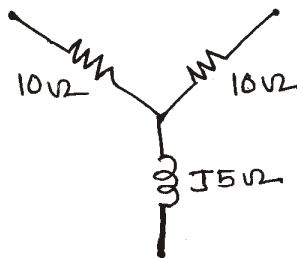


- (b) Convert the given delta-network in to an equivalent star-network :

5

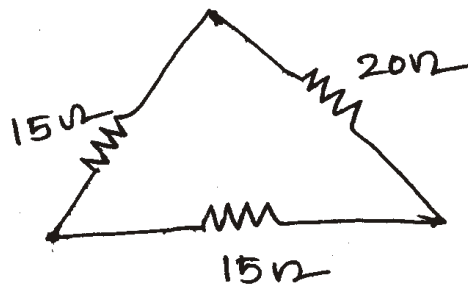


14. (a) Write the mesh current equations for the given network and arrange them in matrix form :

5

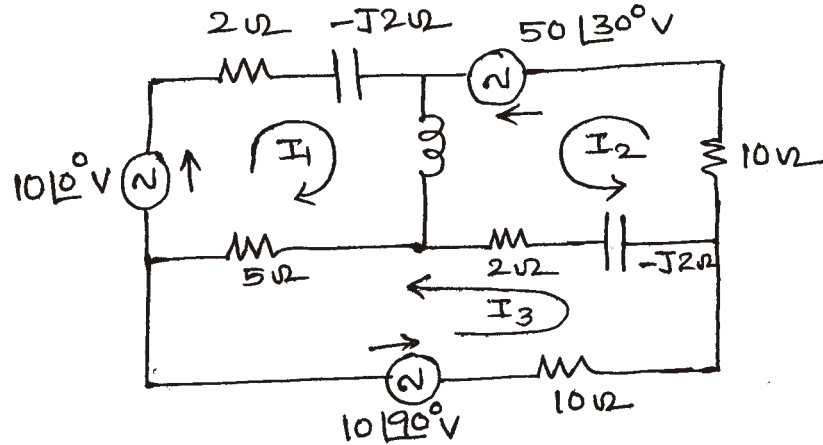


- (b) Apply super mesh techniques to find mesh currents I_1 , I_2 and I_3 for the given network :

5

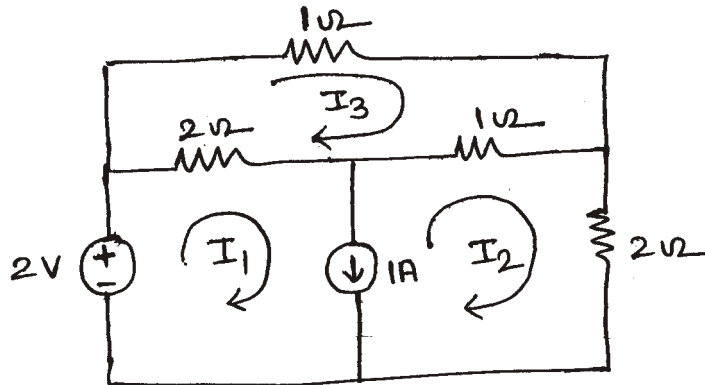


15. Determine node voltages V_1 and V_2 , using Cramer's rule of the given network :

10

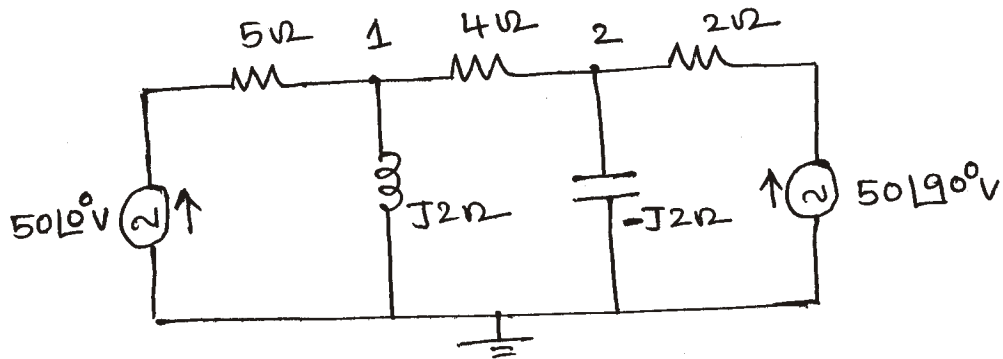

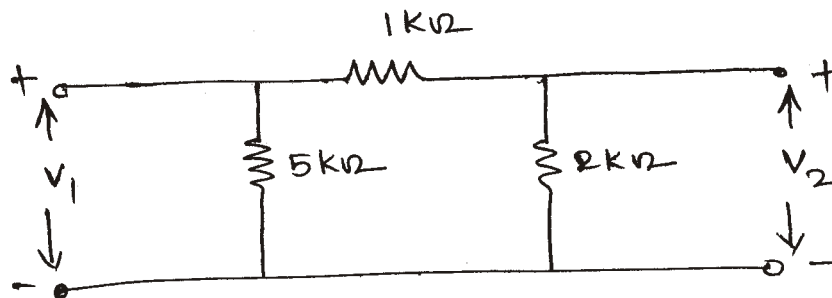16. (a) ^{*} A series R-C circuit with $R = 5000$ and $C = 20 \text{ f}$ has a constant voltage $V = 100$ volts applied at $t = 0$ by closing a switch and capacitor has no initial charge, find the complete current. 5
- (b) Explain how R-C circuit acts as an integrator. 5
17. (a) Explain the short circuit admittance (Y) parameters with equivalent circuit. 5
- (b) Find the Y-parameters for the network shown below : 5



18. (a) Draw the characteristics curves of LPF, HPF, BPF and BSF filters. 4
- (b) Design a T-type attenuator to give 60 db attenuation and to have a line impedance of 500Ω . 6
