



C14-EC-403

4436

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH / APRIL - 2019

DECE - IV SEMESTER EXAMINATION

NETWORK ANALYSIS

Time : 3 Hours]


[Total Marks : 80

PART - A

3×10=30

- Instructions :**
- (1) Answer **ALL** questions.
 - (2) Each question carries **THREE** marks.
 - (3) Answer should be brief and straight to the point and shall not exceed five simple sentences.

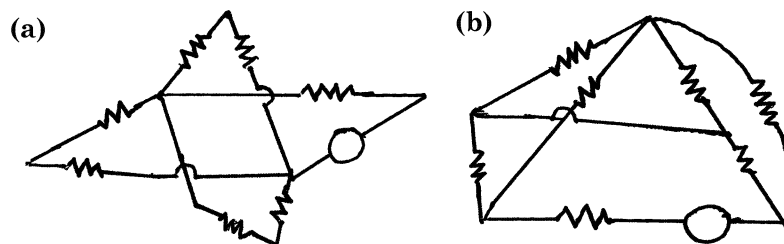- 1 State Kirchhoff's current law.
- 2 List any three applications of tuned circuits.
- 3 State reciprocity theorem.
- 4 List the limitations of Norton's theorem.
- 5 Define the following (a) tree (b) co-tree (c) links.
- 6 Determine the number of nodal equations for the given network.



- 7 Define the terms steady state and transient.
- 8 Give the conditions for symmetry in terms of Z, h and ABCD parameters for a two port network.
- 9 Give the expression for cutoff frequency for constant K-low pass filter and high pass filter.
- 10 Draw the circuits of series and shunt equalizer.

4436]

1


[Contd...

PART - B


10×5=50

- Instructions :**
- (1) Answer any **FIVE** questions.
 - (2) Each question carries **TEN** marks.
 - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

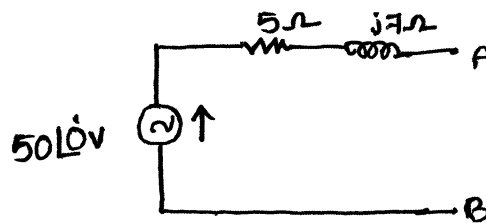
- 11 (a) Explain the dot rule for coupled circuits. 6
- (b) Convert the following voltage source into an equivalent current source. 4



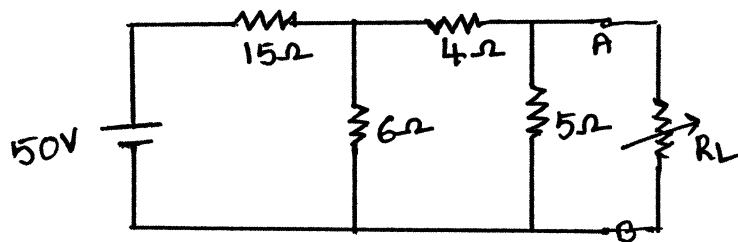
- 12 Determine the maximum power delivered to the load in the circuit shown below. 6+2+2



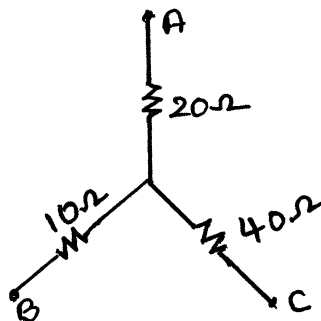
- 13 (a) Find the delta equivalent circuit for given star connected circuit. 5



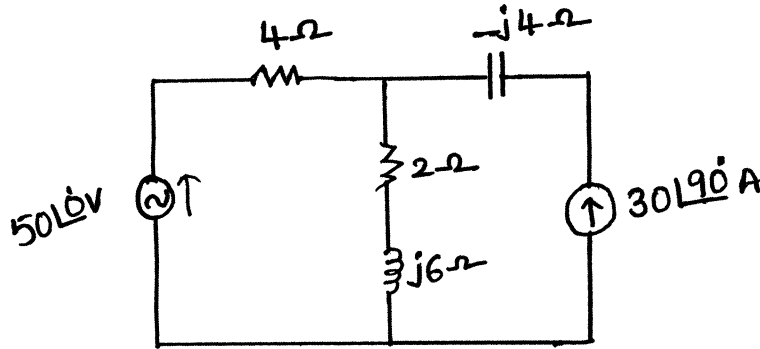
- (b) For the circuit shown below, determine the current in $2 + 2 + 1$
 $(2 + j6)\Omega$ by using superposition theorem.



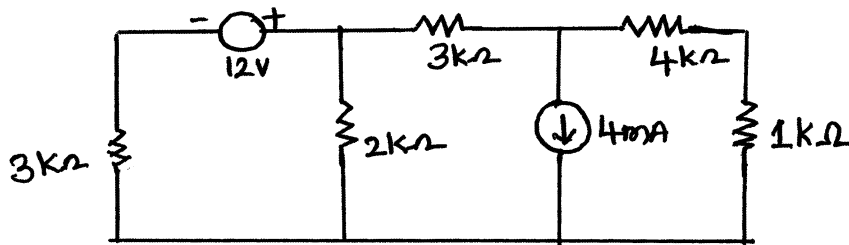
- 14 Find the voltage drop across the $2k\Omega$ resistor by using node analysis technique. 10



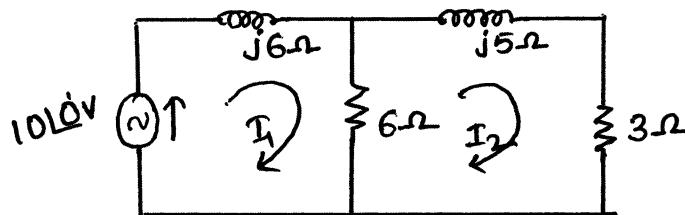
- 15 (a) Write the mesh current equations in the circuit and determine the currents I_1, I_2 7



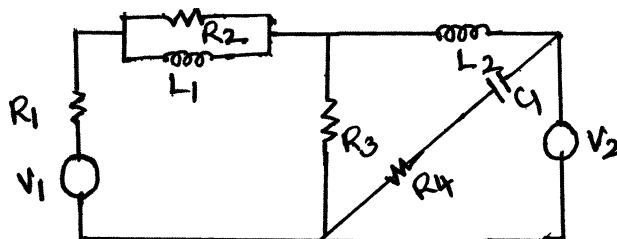- (b) Find the number of mesh equations required to solve the given network. 3



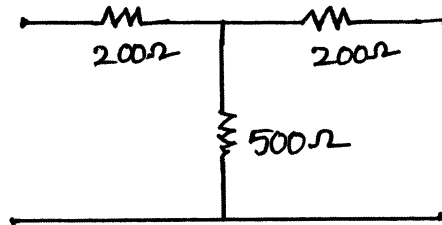- 16 (a) Derive the expression for $i(t)$ and voltage across capacitance $V_c(t)$ for series RC circuit for DC voltage. 7
 (b) Draw the output waveforms of a RC integrator circuit for a square wave input. 1+1+1
- 17 (a) Explain the short circuit admittance (Y) parameters with an equivalent circuit. 6
 (b) Find the Z parameters for given T-network. 4



- 18 (a) Derive the expression for characteristic impedance for δ -network. 6
 (b) Design a δ -type attenuator for given attenuation of 20dB and characteristic impedance of 100Ω . 4