



C14-EC-504

**4630**

**BOARD DIPLOMA EXAMINATION, (C-14)**

MARCH / APRIL - 2019

**DECE - V SEMESTER EXAMINATION**

**MICROCONTROLLER APPLICATIONS**

Time : 3 Hours]

[Total Marks : 80

---

**PART - A**

**3×10=30**

- Instructions :**
- (1) Answer **ALL** questions.
  - (2) Each question carries **THREE** marks.
  - (3) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1 Write about the need for Hardware Interfacing.
- 2 Define the following terms: (a) Resolution (b) Conversion time.
- 3 List any 6 popular UV EPROM chips.
- 4 List various types of Semiconductor Memories used.
- 5 Define the term memory mapped I/O.
- 6 List the features of 8255.
- 7 What are the functions of RTC ?
- 8 Draw the Pin configuration of DS 12887 IC.
- 9 List numbers of 3 commonly used Opto coupler ICs.
- 10 What is the use of PWM for controlling the speed of small DC motor ?

4630 ]

1

[ Contd...

**PART - B****10×5=50**

- Instructions :**
- (1) Answer any **FIVE** questions.
  - (2) Each question carries **TEN** marks.
  - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11** List various types of interfacing devices and mention the functions of each interfacing device.
- 12** (a) Draw and explain the pin diagram of 740LS138  $3 \times 8$  decoder. **5**  
 (b) Explain Memory address decoding 740LS138  $3 \times 8$  decoder. **5**
- 13** (a) Explain the DATA Movement in External RAM using MOVX instruction. **6**  
 (b) Write a program to read 200 bytes of data from P1 and save the data in external RAM location 50000H. **4**
- 14** Draw and explain the interfacing circuit of LCD with 8051.
- 15** (a) Draw and explain the Control word Format (I/O) Mode of 8255. **5**  
 (b) Draw and explain Interfacing circuit of 8051 with 8255. **5**
- 16** (a) With the help a of a circuit diagram, explain the interfacing of DS12887 to 8051. **6**  
 (b) Explain Address map of DS 12887. **4**
- 17** Explain the interrupt and alarm features of DS 12887.
- 18** (a) Explain the application of a temperature controller with the help of a block Diagram. **5**  
 (b) Write an ALP to run stepper motor continuously. **5**