



C-14-EE-405

4444

BOARD DIPLOMA EXAMINATION, (C-14)

MARCH / APRIL - 2019

DEEE - IV SEMESTER EXAMINATION

ELECTRONICS - II

Time : 3 Hours]

[Total Marks : 80

PART - A

3×10=30

- Instructions :**
- (1) Answer **ALL** questions.
 - (2) Each question carries **THREE** marks.
 - (3) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1 Define : (i) Feedback and (ii) Feedback factor.
- 2 Draw the circuit diagram of single tuned amplifier.
- 3 State the conditions required for sustained oscillations in oscillators.
- 4 List any six applications of Oscillator.
- 5 List the characteristics of ideal Operational Amplifier.
- 6 State the need for timer.
- 7 Draw the wave forms of frequency modulated wave.
- 8 Define Frequency modulation and Frequency deviation.
- 9 State the necessity of time base voltage in CRO.
- 10 State the need for A/D convertors.

4444]

1

[Contd...

PART - B

10×5=50

- Instructions :**
- (1) Answer any **FIVE** questions.
 - (2) Each question carries **TEN** marks.
 - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- 11** (a) Distinguish between voltage and power amplifier. **5**
(b) Draw the block diagrams of Voltage series and Voltage Shunt feedback amplifiers. **5**
- 12** Explain the effect of feedback on gain, band width, distortion and noise.
- 13** Explain the working of Colpitts Oscillator with the help of circuit diagram.
- 14** Explain the working of UJT Relaxation Oscillator with the help of circuit diagram.
- 15** Explain the Operation Amplifier as :
(i) Summer (ii) Integrator
(iii) Differentiator (iv) Inverter.
- 16** Draw and explain the internal block diagram of IC555 timer.
- 17** (a) Explain the effect of Over modulation and Under modulation in AM with waveforms. **5**
(b) Compare AM and FM systems. **5**
- 18** Explain A/D conversion using successive approximate method.