



C14-EE-505

**4637**

**BOARD DIPLOMA EXAMINATION, (C-14)**

MARCH / APRIL - 2019

**DEEE - V SEMESTER EXAMINATION**

**DIGITAL ELECTRONICS**

Time : 3 Hours]

[Total Marks : 80

---

**PART - A**

**3×10=30**

**Instructions :**

- (1) Answer **ALL** questions.
- (2) Each question carries **THREE** marks.
- (3) Answer should be brief and straight to the point and shall not exceed five simple sentences.

- 1 Convert 736.65<sub>(8)</sub> octal number in to binary number system.
- 2 State and explain de-Morgan's theorems.
- 3 Define the terms : (i) fan-in (ii) fan-out.
- 4 Draw the diagram of TTL NAND gate with totempole output.
- 5 Draw the logic circuit of half adder using EX-OR and AND gates, give its truth table.
- 6 State the need for tri-state buffer, draw its symbol.
- 7 Compare TTL, CMOS, ECL logic families.
- 8 Explain NOR latch with truth table.
- 9 What is race around condition ?
- 10 Distinguish between NVRAM and flash ROM.

4637 ]

1

[ Contd...

**PART - B****10×5=50**

- Instructions :**
- (1) Answer any **FIVE** questions.
  - (2) Each question carries **TEN** marks.
  - (3) Answer should be comprehensive and the criterion for valuation is the content but not the length of the answer.

- |           |  |            |
|-----------|--|------------|
| <b>11</b> | Draw the NOT, AND, OR gates using NAND, NOR gates only.                        | <b>10</b>  |
| <b>12</b> | Draw and explain TTL NAND gate open collector type circuit.                    | <b>10</b>  |
| <b>13</b> | (a) Define (i) propagation delay (ii) power dissipation<br>(iii) noise margin. | <b>3×2</b> |
|           | (b) Draw the circuit of CMOS NAND gate circuit.                                | <b>4</b>   |
| <b>14</b> | Draw and explain 4-bit parallel adder circuit.                                 | <b>10</b>  |
| <b>15</b> | (a) Draw and explain 4×2 encoder circuit.                                      | <b>7</b>   |
|           | (b) Draw the circuit of 2×4 decoder circuit.                                   | <b>3</b>   |
| <b>16</b> | Explain the operation of master – slave JK flip flop with neat diagram.        | <b>10</b>  |
| <b>17</b> | Explain the operation and decade counter.                                      | <b>10</b>  |
| <b>18</b> | Explain a simple diode ROM.  | <b>10</b>  |