



C16-EE-402

5655

BOARD DIPLOMA EXAMINATION, (C-16)
MARCH/APRIL—2018
DEEE—FOURTH SEMESTER EXAMINATION

AC MACHINES—I

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

Instructions : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Explain why the transformer should not be connected to DC supply.
2. Distinguish between core-type and shell-type transformers.
3. Draw the vector diagram of single-phase transformer on no-load.
4. Define all-day efficiency and commercial efficiency of a single-phase transformer.
5. State any three advantages of three-phase transformer over a bank of three single-phase transformers.
6. State the methods of cooling a transformer.
7. Briefly explain the working principle of alternator.

/5655

*

1

[Contd...

8. What are the advantages of stationary armature over rotating-type armature?
9. Define (a) synchronous reactance and (b) synchronous impedance of an alternator.
10. State the conditions for parallel operation of alternator.

PART—B

10×5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. With neat sketch, explain the construction and working of a single-phase transformer.

12. A 220/440 V, single-phase transformer has the following particulars :

$$R_1 = 0.5, X_1 = 1.8, R_2 = 0.5 \text{ and } X_2 = 3$$

Calculate the total impedance of the transformer referred to primary and secondary.

13. A 10 kVA, 2500/250 V, 50 Hz, 1- transformer gave the following test results :

OC test : 250 V, 0.8 A and 50 W

SC test : 60 V, 3 A and 45 W

(a) Calculate the efficiency at $\frac{1}{4}$, $\frac{1}{2}$ of the full load at 0.8 p.f. lag.

(b) Calculate the load in kVA at the maximum efficiency.

14. (a) ^{*}Distinguish between distribution transformer and power transformer.
(b) Derive the condition for maximum efficiency.
15. Draw the connection diagrams of (a) star-star, (b) delta-delta, (c) star-delta and (d) delta-star configurations of 3- transformers.
16. (a) Derive the e.m.f. equation of an alternator.
(b) Obtain the relation between no-load EMF and terminal voltage in alternator.
17. A 200 kVA, 415 V, 50 Hz, 3- alternator has effective armature resistance of 0.01 and an armature leakage reactance of 0.05 . Compute the voltage induced in the armature winding when the alternator is delivering rated current at a load power factor of (a) 0.8 lag and (b) 0.8 lead.
18. Explain the procedure of synchronisation by using lamp method.

*